

## Coding Challenge 4.0

---

### Problem: R wela 1/R.

#### Statement

Kratos, the God of War, has been tasked with a circuit analysis challenge. His goal is to determine the equivalent resistance value of a circuit composed of resistors connected in series and parallel. The circuit is represented as a string of resistor values, and the following notations are used:

`[]`: Indicates that all the available resistors are connected in parallel.

`()`: Indicates that all the available resistors are connected in series.

**The equivalent resistance value for resistors connected in series:**

is calculated as follows:  $R_{eq} = R_1 + R_2 + \dots + R_n$ .

**The equivalent resistance value for resistors connected in parallel:**

is calculated as follows:  $1/R_{eq} = 1/R_1 + 1/R_2 + \dots + 1/R_n$ .

Note that all resistance values are positive and expressed in ohms and fixed with two digits after the , in float cases.

Kratos must use his expertise in circuit analysis to compute the equivalent resistance value of the circuit. Will he succeed and emerge victorious once again?

## Examples :

Input	Output
(10, [20, 30])	22.00
((5, [10, 2]), ([20, 30], 10, [20, 40]))	42.00
(10, 5, 16, [(16, 14), [(15, 10), 5]])	34.66
(5, 8, 9, [10, 24])	29.06